

# CONTROL SYSTEMS

G.VARSHIT  
EE19BTECH11020

September 6, 2020

Question

Theoretical background

Solution

Solution(a)

Solution(b)

## Question

- Find the transfer function  $G(s) = V_o(s)/V_i(s)$ , for each operational amplifier circuit shown in figures given below

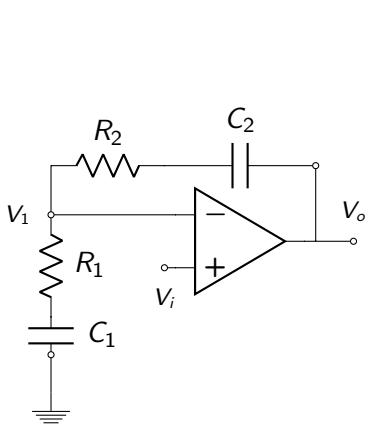


Fig.(a)


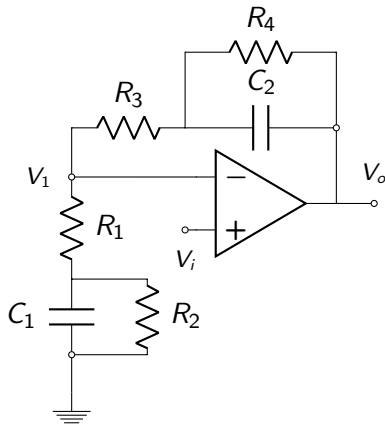


Fig.(b)
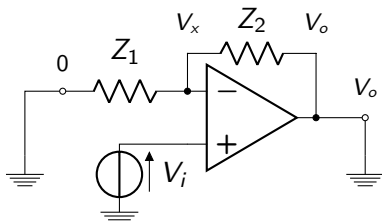
## Non Inverting Op-Amp

General Non Inverting Op-Amp is as follows:



Using the voltage divider rule in above circuit :

$$V_x = \frac{Z_1}{Z_1 + Z_2} * V_o \quad (2.1)$$

As the ideal op-amp's input impedance is infinite, its positive and negative terminal are virtually short

$$V_+ = V_- \quad (2.2)$$

## TRANSFER FUNCTION of Non Inverting Op-Amp

From the above circuit we know:

$$V_+ = V_i \text{ and } V_- = V_x \quad (2.3)$$

So from Eq.(2.2) and Eq.(2.3), this implies

$$V_i = V_x$$

From Eq.(2.1):

$$V_i = \frac{Z_1}{Z_1 + Z_2} * V_o$$
$$\boxed{\frac{V_o}{V_i} = \frac{Z_1 + Z_2}{Z_1}} \quad (2.4)$$

We apply this formula of transfer function of Non inverting Op-amp [Eq.(2.4)] in Fig.(a) and Fig.(b) to obtain solution.

## Resistor and Capacitor values for Fig.(a)

Here in Fig.(a), resistor and capacitor values are given as following:

- $R_1 = 4 \cdot 10^5 \Omega$
- $C_1 = 4 \cdot 10^{-6} \text{ F}$
- $R_2 = 1.1 \cdot 10^5 \Omega$
- $C_2 = 4 \cdot 10^{-6} \text{ F}$

Hence comparing with general terms :

1. Impedance  $Z_1$  is given by series combination of resistance  $R_1$  and capacitance  $C_1$
2. Impedance  $Z_2$  is given by series combination of resistance  $R_2$  and capacitance  $C_2$



## Calculating $Z_1$ and $Z_2$ for Fig.(a)

We know Impedance of Capacitor(C) in Laplace form =  $\frac{1}{sC}$ .

Hence, :

$$Z_1(s) = R_1 + \frac{1}{sC_1}$$

$$Z_1(s) = 4 * 10^5 + \frac{1}{4s * 10^{-6}} \quad (3.1)$$

$$Z_2(s) = R_2 + \frac{1}{sC_2}$$

$$Z_2(s) = 1.1 * 10^5 + \frac{1}{4s * 10^{-6}} \quad (3.2)$$



## Solution(a)

From Eq.(2.4) :

$$G(s) = \frac{V_o(s)}{V_i(s)} = \frac{Z_1 + Z_2}{Z_1}$$

From Eq.(3.1) and Eq.(3.2):

$$G(s) = \frac{(4 * 10^5) + (1.1 * 10^5) + \frac{1}{4s * 10^{-6}} + \frac{1}{4s * 10^{-6}}}{4 * 10^5 + \frac{1}{4s * 10^{-6}}}$$

Therefore on further simplification:

$$G(s) = \frac{51s + 50}{40s + 25}$$

$$G(s) = 1.275 \left( \frac{s + 0.98}{s + 0.625} \right)$$



## Resistor and Capacitor values for Fig.(b)

Here in Fig.(a), resistor and capacitor values are given as following:

- $R_1 = 4 \cdot 10^5 \, \Omega$
- $C_1 = 4 \cdot 10^{-6} \, \text{F}$
- $R_2 = 6 \cdot 10^5 \, \Omega$
- $R_3 = 6 \cdot 10^5 \, \Omega$
- $C_2 = 4 \cdot 10^{-6} \, \text{F}$
- $R_4 = 1.1 \cdot 10^5 \, \Omega$

Hence comparing with general terms :

1. Impedance  $Z_1$  is given by series combination of resistance  $R_1$  and another impedance which is parallel combination of  $R_2$  and  $C_1$
2. Impedance  $Z_2$  is given by series combination of resistance  $R_3$  and another impedance which is parallel combination of  $R_4$  and  $C_2$



## Calculating $Z_1$ and $Z_2$ for Fig.(b)

We know Impedance of Capacitor(C) in Laplace form =  $\frac{1}{sC}$ .

Hence, :

$$Z_1(s) = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{\frac{1}{sC_1}}} = R_1 + \frac{R_2}{sR_2C_1 + 1}$$

$$Z_1(s) = 4 * 10^5 + \frac{6 * 10^5}{6s * 10^5 * 4 * 10^{-6} + 1} \quad (3.3)$$

$$Z_2(s) = R_3 + \frac{1}{\frac{1}{R_4} + \frac{1}{\frac{1}{sC_2}}} = R_3 + \frac{R_4}{sR_4C_2 + 1}$$

$$Z_2(s) = 6 * 10^5 + \frac{1.1 * 10^5}{1.1s * 10^5 * 4 * 10^{-6} + 1} \quad (3.4)$$

## Solution(b)

From Eq.(2.4) :

$$G(s) = \frac{V_o(s)}{V_i(s)} = \frac{Z_1 + Z_2}{Z_1}$$

From Eq.(3.3) and Eq.(3.4):

$$G(s) = \frac{(4 * 10^5) + (6 * 10^5) + \frac{6*10^5}{6s*10^5*4*10^{-6}+1} + \frac{1.1*10^5}{1.1s*10^5*4*10^{-6}+1}}{4 * 10^5 + \frac{6*10^5}{6s*10^5*4*10^{-6}+1}}$$

Therefore on further simplification:

$$G(s) = \frac{10.56s^2 + 33.68s + 17.1}{4.224s^2 + 14s + 10}$$

$$G(s) = \frac{2640s^2 + 8420s + 4275}{1056s^2 + 3500s + 2500}$$